

CLASS: XI - H/J/M/K
DATE: 23/11/2022

4 marks

- 6 marks**

- 6 marks**

- 4 marks**

- 6 marks**

1. Define alpha and beta of a transistor.
2. Draw the symbols of PNP and NPN transistors.
3. In a common base connection, $I_C = 0.95 \text{ mA}$ and $I_B = 0.05 \text{ mA}$. Find the value of α .

Q3 B. Answer any one of the following.

4 marks

1. Explain N type semiconductor in short.
2. Draw the circuit diagram for studying the characteristics of a transistor.

Q4 A. Answer any two of the following.

6 marks

1. Define input and output characteristics of a transistor.
2. What are semiconductors? What is negative temperature coefficient of resistance?
3. What is intrinsic semiconductor?

Q4 B. Answer any one of the following.

4 marks

1. Derive the relation between α and β for a transistor.
2. In a CE transistor circuit if $\beta=100$ and $I_B=50\mu A$. Compute the values of α , I_E and I_C .

Q5 A. Answer any two of the following.

6 marks

1. How does current flow in an intrinsic semiconductor?
2. Write any three postulates of Bohr's atomic model.
3. Explain the structure of transistors.

Q5 B. Answer any one of the following.

4 marks

1. Explain the output characteristics of a transistor with necessary diagrams.
2. Explain the common base and common emitter configuration of the transistor