

Code: A-E616116-M

I SEMESTER EXAM – 2025-26

2 x 75

Std.: XI

Sub: ELECTRICAL MAINTENANCE-I

Marks: 40

Date:

Roll No.: _____

Time: 2½ Hrs.

Q.1 Fill in the blanks. (any four)

4

- a)  is the symbol of _____.
- i. Capacitor ii. Choke iii. Inductor
- b) _____ effect of electric current is used in an electroplating.
- i. Chemical effect ii. Physical effect iii. Heating effect
- c) In First angle projection method, the Left Hand Side View is drawn on _____ side of the Front View.
- i. Left hand ii. Right hand iii. Top
- d) The fuse is connected in _____ wire.
- i. phase ii. neutral iii. earth
- e) _____ is defined as the rate of doing work.
- i. Electrical Power ii. Electrical Energy iii. Electrical work done
- f) Fuses, MCBs are _____ devices.
- i. Safety ii. Controlling iii. Consuming

Q.2 Attempt any two

4

- a) Draw symbols of the following:
- i. Horn
- ii. Socket outlet, 3 pin 15A
- iii. Main fuse board with switches, power
- iv. Earth
- b) Draw a neat and labelled circuit diagram of staircase wiring.
- c) Draw a neat and labelled circuit diagram of one-point series parallel testing board.

Q.3 Attempt any three

6


- a) Draw a neat and labelled circuit diagram of Godown wiring.
- b) State the different effects of electric current.
- c) Draw a neat and labelled circuit diagram of 2-point Extension board.
- d) Draw symbols of the following:
- i. Single phase Energy Meter
- ii. AC Motor
- iii. Buzzer
- iv. Fixed Resistance

Q.4 Attempt any four

12

- a) Define:
- i. Terminal Voltage
- ii. Electric Energy
- iii. Conductance
- b) Compare Series and Parallel circuits.
- c) Two lamps of 200 W each are connected in i) parallel & ii) series to a 220 Volt supply. Calculate the power taken in each case.

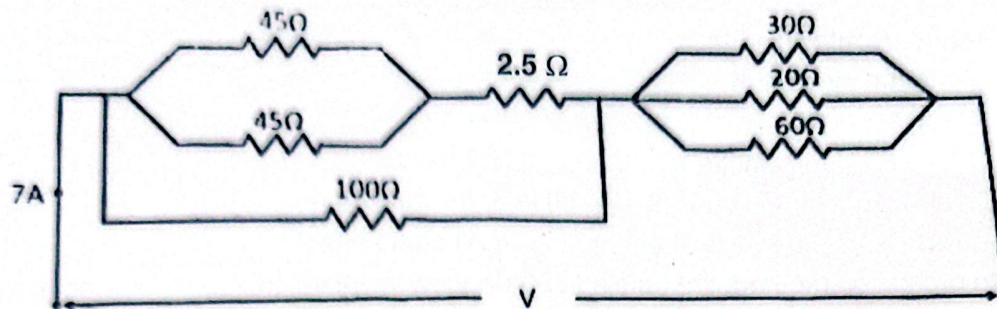- d) Find the equivalent resistance of the circuit below. If the current passing through it is 7A, find the voltage, of supply.



- e) State and explain the laws of resistance.

Q.5 The electrical installation in a house is used in the following manner.

- Lamp 100 W each, 12 nos. 8 hrs a day
- Fan 60 W each, 8 nos. 7 hrs a day
- Electric cooker 1 KW each, 2 nos. 5 hrs a day
- Electric Geyser 1.5 KW each, 2nos. 3 hrs a day

Calculate the cost of electric energy for the month of October, @ Rs.4.50 per unit.

Q.6 Draw the Front View, Top View and Side View of the figure given below, in First Angle Projection Method.

