

Code: A-E223115-A

I SEMESTER EXAM - 2024-25

2 x 155

Std.: XI

Sub: Electrical Maintenance - I

Marks: 40

Date:

Roll No.: _____

Time: 2½ hrs.

Q.1 Fill in the blanks with correct options.

(6)

- a)  is the symbol of
i) Capacitor ii) Variable resistance iii) Inductor
- b) effect of electric current is used in electric iron.
i) Chemical ii) Physical iii) Heating
- c) wires retain their shape even after bending and twisting.
i) VIR ii) Weather-proof iii) Flexible
- d) The fuse is connected in _____ wire.s
i) phase ii) neutral iii) earth
- e) The resistance of an electric heater is _____ when it takes a current of 5A at 250V supply.
i) 25Ω ii) 50Ω iii) 5Ω
- f) _____ wires are used for outdoor wiring.
i) Weatherproof ii) VIR iii) CTS / TRS

Q.2 Attempt any three.

(6)

- a) Draw symbols of the following.
i) Bell ii) D.O.L. starter iii) Earth fault
iv) Siren
- b) Draw a neat and labelled diagram of staircase wiring.
- c) State the different types of wires.
- d) Draw a neat and labelled diagram of one point series parallel testing board.

Q.3 Attempt any four.

(8)


- a) Draw a neat and labelled circuit diagram of Godown wiring.
- b) Write a note on PVC wires with diagram.
- c) Explain plug and socket with diagram.
- d) A voltage of 500V is applied across a load which takes a current of 50 Amps. Find the resistance of the load.
- e) Draw symbols of the following :
i) Battery ii) Kit-Kat fuse
iii) DC series motor iv) AC Generator

Q.4 Attempt any five.

(15)

- a) Compare series and parallel circuit.
- b) Explain the factors on which resistance of material depends.
- c) State the different types of switches and give their applications.
- d) State the effects of electric current and explain any one in detail.

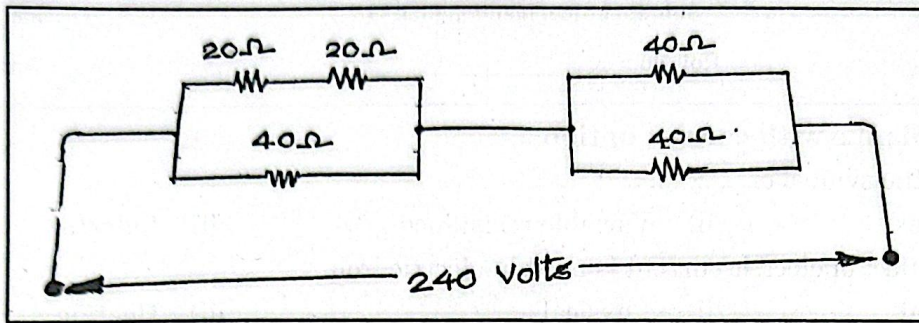- e) Calculate the total resistance and total current in the circuit given below.



- f) Define power. Two lamps of 100 W each are connected. (i) in series (ii) Parallel. Find out the current in each case. Take the supply voltage 250 V in both cases consider voltage rating of lamps 250V.

Q.5 Calculate the energy consumption for the month of October for the following load.

(5)

Find the bill @ Rs 3.50 per unit.

- Two lamps each of 100W working 4 hrs a day.
- Electric heater of 1KW working 2 hrs a day.
- Fan 60W each, 6 nos. working 5 hrs a day.
- Electric cooker 1.5 KW each, 2 nos., 4 hrs a day.