

Code: A-E223115-M

I SEMESTER EXAM – 2024-25

2 x 50

Std.: XI

Sub: ELECTRICAL MAINTENANCE-I

Marks: 40

Date:

Roll No.: _____

Time:

Q.1 Fill in the blanks with correct options.**(06)**

- a)  is the symbol of _____.
- i. Capacitor ii. Variable resistance iii. Inductor
- b) _____ effect of electric current is used in electric Iron.
- i. Chemical ii. Physical iii. Heating
- c) _____ wires retain their shape even after bending and twisting.
- i. VIR ii Weather-proof li. Flexible
- d) The fuse is connected in _____ wire.
- i. phase ii. neutral iii. earth
- e) The resistance of an electric heater is _____ when it takes a current of 5A at 250V supply.
- a) 25 Ω b) 50 Ω c) 5 Ω
- f) _____ wires are used for outdoor wiring.
- a) Weatherproof b) VIR c) CTS/TRS

Q.2 Attempt any three**(06)**


- a) Draw symbols of the following.
- 1) Fixed Resistance 2) Inductive coil 3) Earth fault 4) Lamp in Parallel
- b) Draw a neat and labelled diagram of staircase wiring.
- c) State the different types of wires.
- d) Draw a neat and labelled diagram of one point series parallel Testing board.

Q.3 Attempt any four.**(08)**

- a) Draw a neat and labelled circuit diagram of Godown wiring.
- b) Write a note on VIR wires with diagram.
- c) Explain plug and socket with diagram.
- d) A voltage of 250V is applied across a load which takes a current of 65 Amps. Find the resistance of the load.
- e) Draw symbols of the following,
- (i) Battery (ii) Kit-kat fuse (iii) DC series motor (iv) AC Generator

Q.4 Attempt any five**(15)**

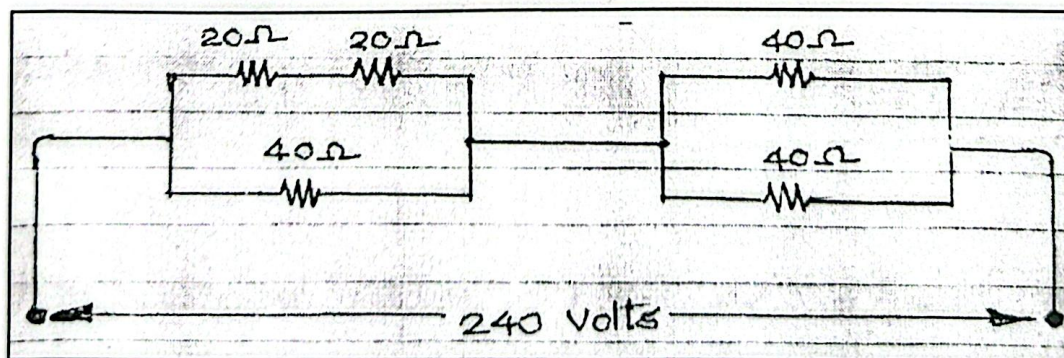- a) Compare Series and Parallel circuit.
- b) Explain the factors on which resistance of the materials depends?
- c) State the different types of the switches and give their applications.
- d) State the effects of electric current and explain any one in detail.
- e) Calculate the total resistance and total current in the circuit given below.



P.T.O

- f) Define power. Two lamps of 100 W each are connected (i) in series (1) parallel. Find out the current in each case. Take the supply voltage 250 V in both cases. Consider voltage rating of lamps 250V.

Q.5 Calculate the energy consumption for the month of October for the following load. **(05)**

Find the bill @ Rs. 4.50 per unit.

- (i) Two lamps each of 100 W working 4 hrs a day.
 - (ii) Electric heater of 1KW working 2 hrs a day.
 - (iii) Fan 60W each, 6 nos. working 5 hrs a day.
 - (iv) Electric cooker 1.5 KW each, 2 nos, 4 hrs a day.
-