

Code: A-E616113-A

I SEMESTER EXAM – 2025-26

2 x 90

Std.: XI

Sub: ELECTRICAL MAINTENANCE-I

Marks: 40

Date: _____

Roll No.: _____

Time: 2½ Hrs.

Q.1 Fill in the blanks. (any four)

4

- a)  is the symbol of _____.
i. Capacitor ii. Choke iii. Inductor
- b) If any one of the supply wires is disconnected, then the circuit is called _____.
i. An open circuit ii. A short circuit iii. A leakage circuit
- c) In First angle projection method, the Right Hand Side View is drawn on _____ side of the Front View.
i. Left hand ii. Right hand iii. Top
- d) The switch is connected in _____ wire.
i. phase ii. neutral iii. earth
- e) _____ is defined as the capacity of doing work.
i. Electrical Power ii. Electrical Energy iii. Electrical work done
- f) _____ effect of electric current is used in an electroplating.
i. Chemical effect ii. Physical effect iii. Heating effect

Q.2 Attempt any two

4

- a) Draw symbols of the following:
i. Hooter
ii. Socket outlet, 3 pin 15 A with switch
iii. Main fuse board with switches, Lighting
iv. Fault
- b) Draw a neat and labelled circuit diagram of staircase wiring,
- c) Draw a neat and labelled circuit diagram of two-point series parallel testing board.

Q.3 Attempt any three

6


- a) Draw a neat and labelled circuit diagram of Godown wiring,
- b) State the different effects of electric current,
- c) Draw a neat and labelled circuit diagram of 2-point Extension board,
- d) Draw symbols of the following:
i. Tachometer
ii. DC shunt Motor
iii. Buzzer
iv. Variable Inductor

Q.4 Attempt any four

12

- a) Define:
i. Terminal Voltage
ii. Electric Power
iii. Conductance
- b) Compare Series and Parallel circuits.
- c) Two lamps of 200 W each are connected in i) parallel & ii) series to a 220 Volt supply. Calculate the power taken in each case.

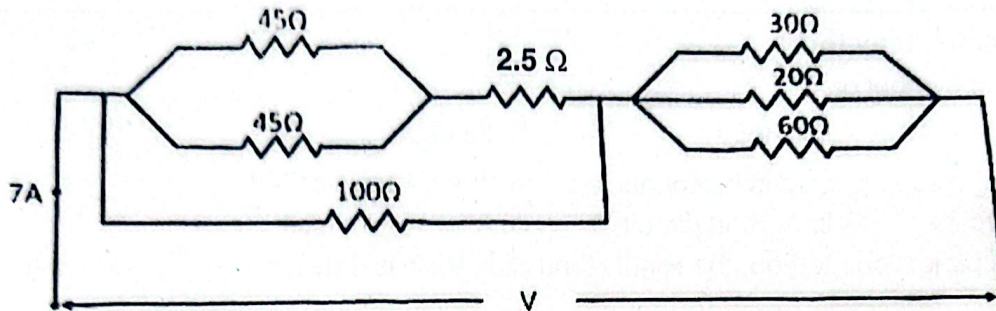- d) Find the equivalent resistance of the circuit below. If the current passing through it is 7A, find the voltage of supply.



- e) State and explain the laws of resistance.

Q.5 The electrical installation in a house is used in the following manner.

5

- Lamp 100 W each, 12 nos. 8 hrs a day
 - Fan 60 W each, 8 nos. 7 hrs a day
 - Electric cooker 1 KW each, 2 nos. 5 hrs a day
 - Electric Geyser 1.5 KW each, 2nos. 3 hrs a day
- Calculate the cost of electric energy for the month of October, @ Rs.4.50 per unit.

Q.6 Draw the Front View, Top View and Side View of the figure given below, in First Angle Projection Method.

9

